

Introductory Lecture

Electronics Club



A short description of

BINARY NUMBER SYSTEM

Binary Number System

- Just another method of describing numbers
- Contains only 0s and 1s
- Conversion from binary to normal (decimal) system
- Conversion from normal to binary system

An introduction

DIGITAL ELECTRONICS

What is “Digital Electronics”?


- Consists of only two states: LOW and HIGH
- LOW corresponds to 0V, and HIGH corresponds to 5V (approx.)
- Signals work as binary numbers, LOW stands for 0, and HIGH stands for 1.
- Can use boolean algebra on electronic signals to perform operations and calculations.

Why?


- Easier to design
- Less chance of errors due to voltage fluctuations
- Others...

Tools of the trade

Breadboards

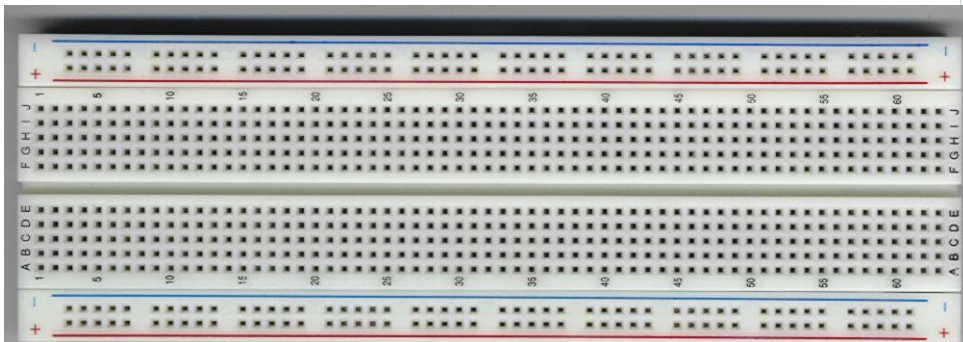

Integrated circuits

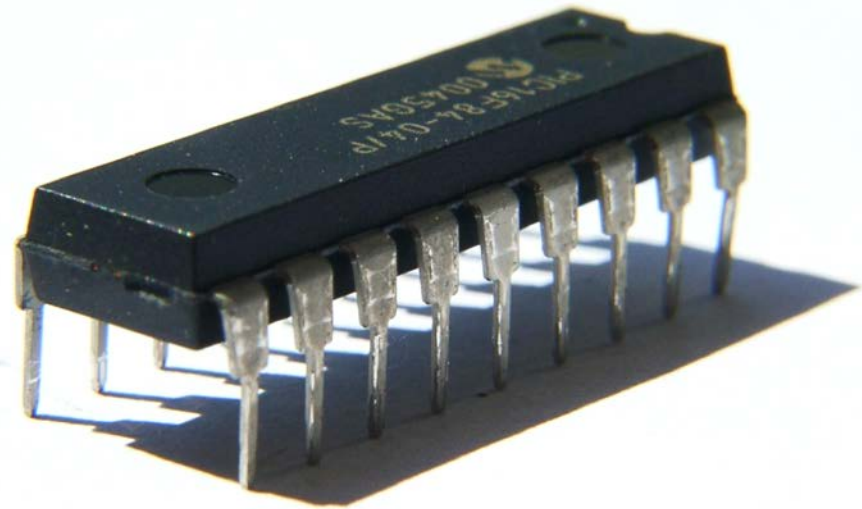

Let's get started!


PROBLEM STATEMENT

“Design a circuit that counts the number of times a button is pressed.”

What do we need?


- A button
- Something that counts and stores the number of times the button has been pressed
- A display

Meet the button

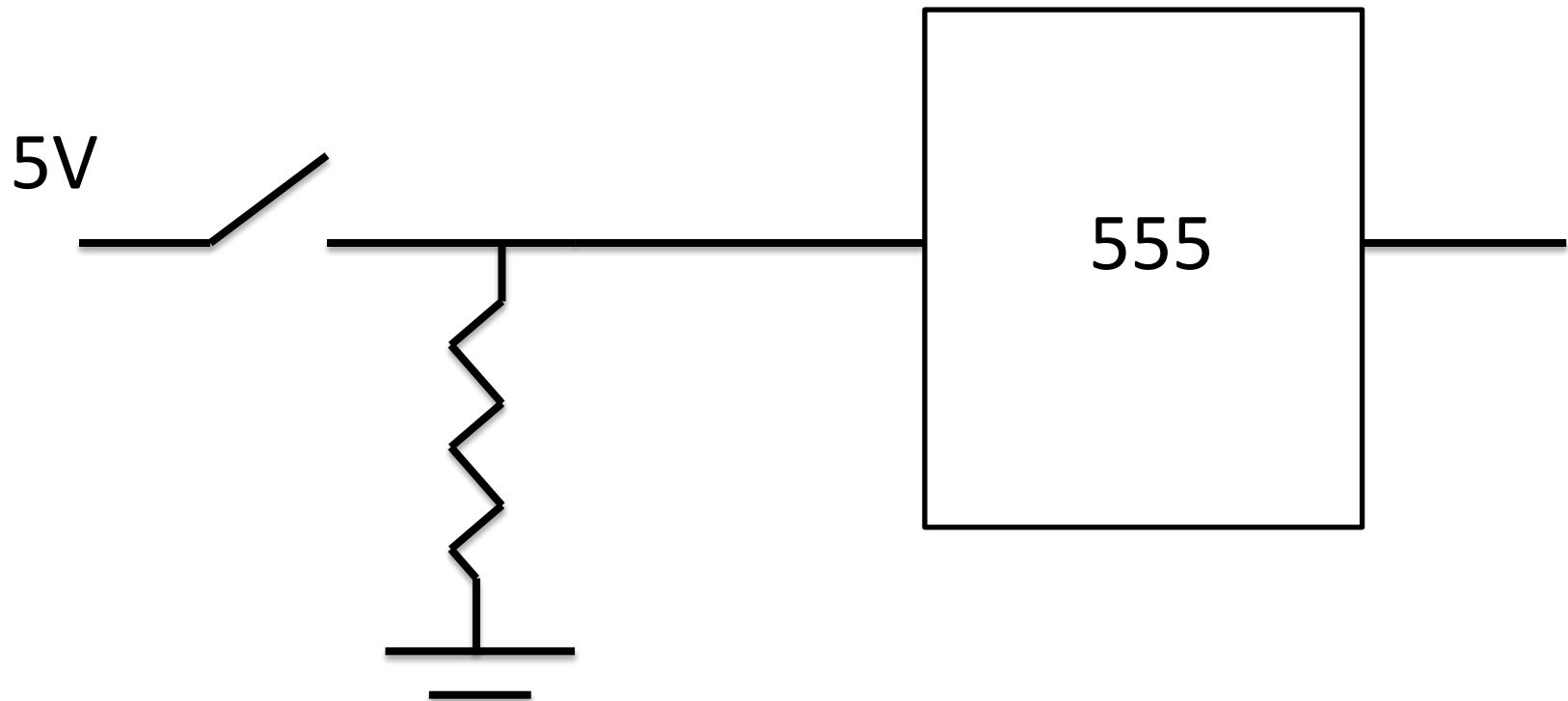



How do we count?

Using a 4029 counter

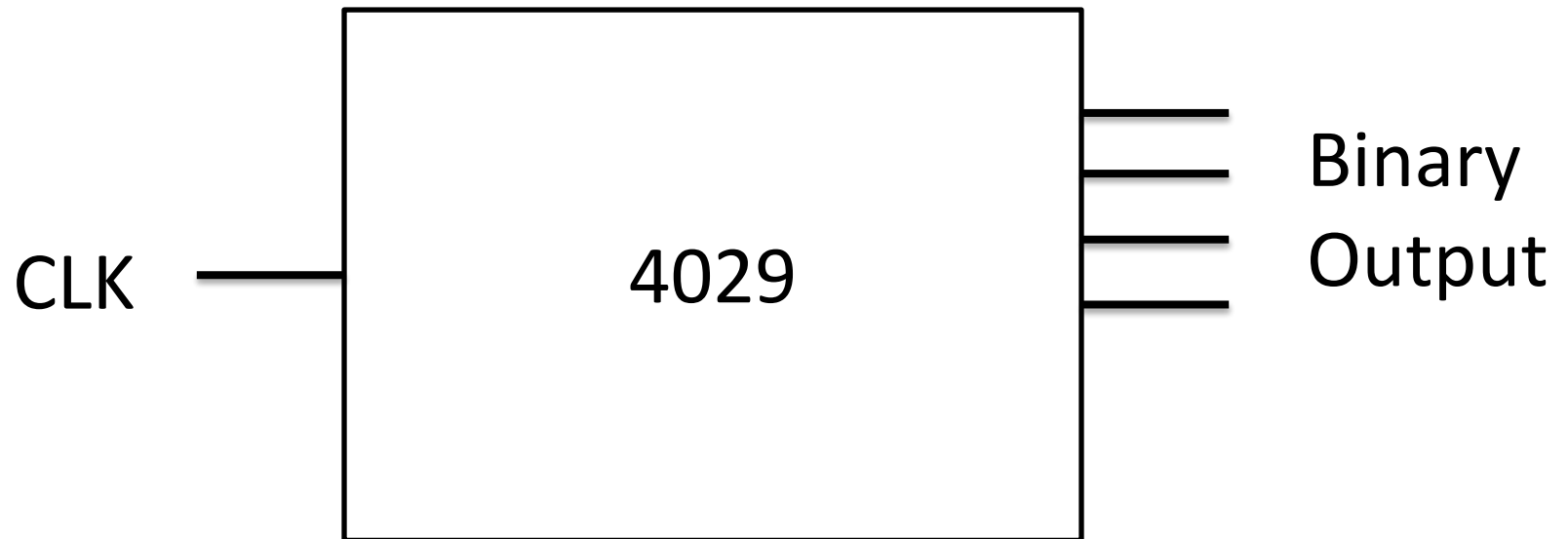


Time to display

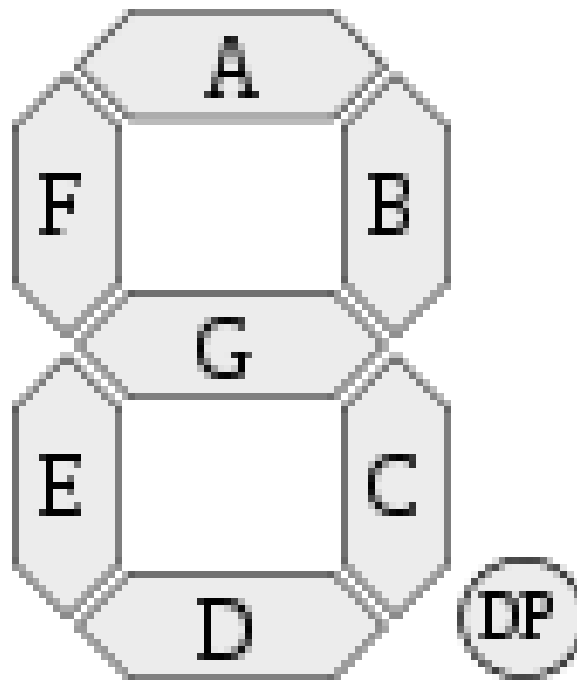

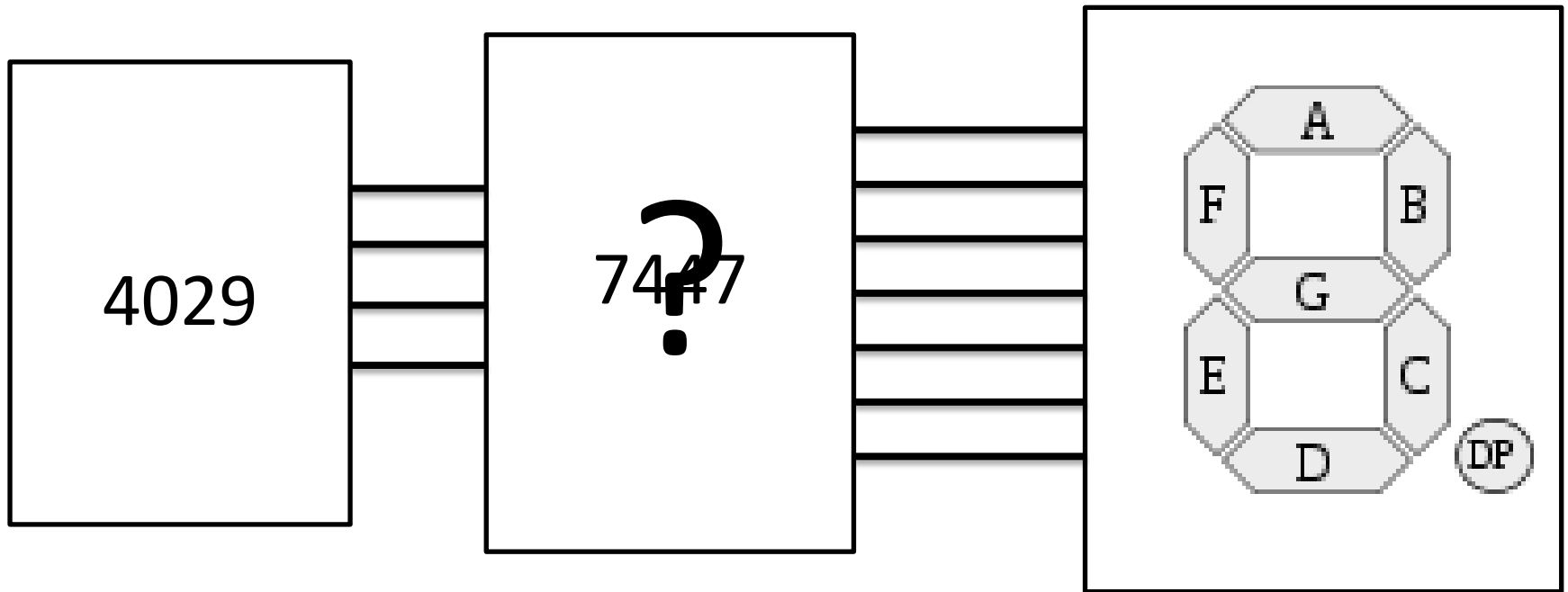

Final Circuit

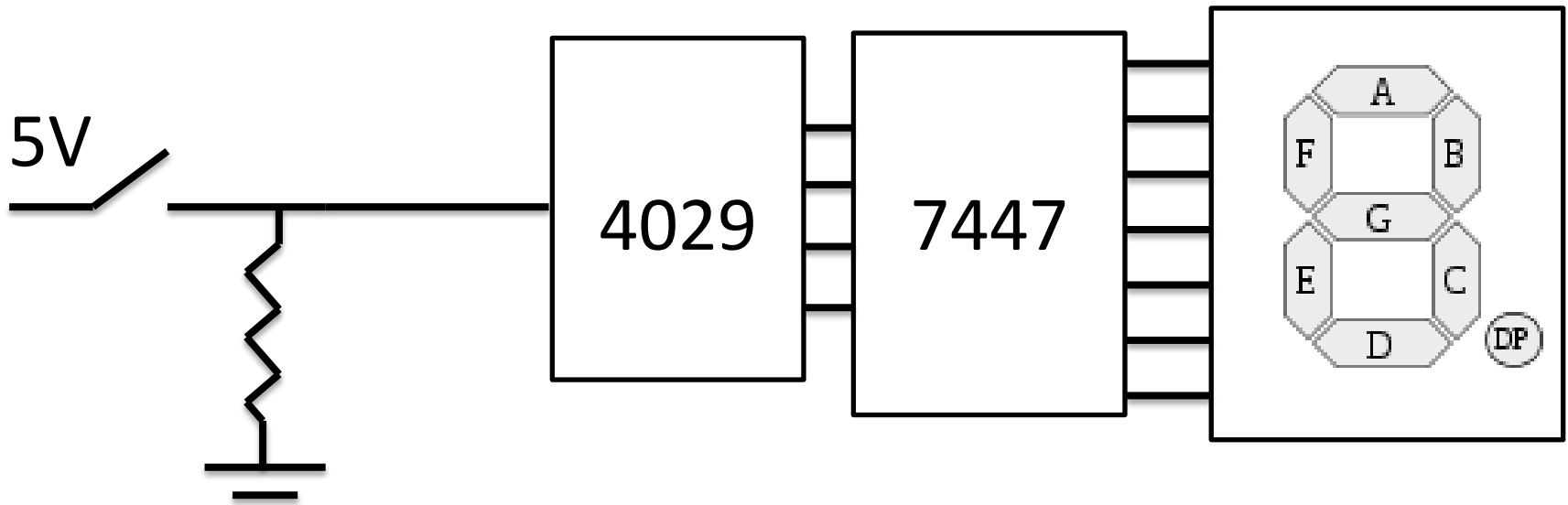

See you at the workshop!

- Workshop slots will be conveyed shortly
- YOU will implement the circuit
- We will look at some other interesting facts and features about the ICs

Parting remarks

- Website: students.iitk.ac.in/eclub
- E-mail: eclub.iitk@gmail.com

Thank you!

Abhinav Prateek

Chirag Sangani

Sumeet Kumar